

ADC Using 8051 (Trainer: Dr. Jeevan K M)

AVVA PRAVEEN BABU

BU21EECE01000527

Learning Objective:

- Using the ADC 0808, you will be able to comprehend the transformation of an analog signal into a digital one.
- This chapter will focus on incorporating the ADC 0808 with the 8051 microcontroller.

Inputs and Outputs:

• \square **Input:** A potentiometer (1k or 10k ohms).

• □ **Outputs:** LEDs.

Logic:

- The ADC 0808 uses one of its input channels for the analog output of the potentiometer.
- The microcontroller Port 1 has connected digital output pins (D0-D7) from the ADC0808.
- On the other hand, to select an input channel, the ADC selection lines (A, B, C) are all attached to the port 2 of 8051.
- Moreover, additional control lines such as End of Conversion (EOC), Start etc. are also connected to this port.
- Port 3 of 8051 houses LEDs which displays digital value read out by a potentiometer.
- Thus, depending on variation in resistance caused by a potentiometer, the state of LEDs at port three will change drastically hence effecting transformation in D.V.O outputted by the ADC

Results:-



